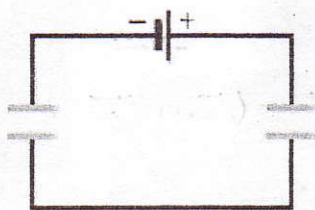


You should know how to compute the energy stored in a capacitor, given either its charge or potential difference. You should also know how to compute the energy density at points between the plates or, in general, at any point within a given electric field.

## Questions and Example Problems from Chapter 25


### Question 1

For each circuit in the figure below, are the capacitors connected in series, in parallel, or in neither mode?




(a)

series

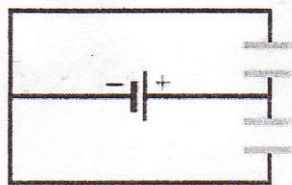

(b)

parallel

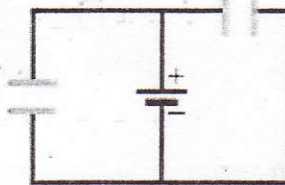


(c)


parallel
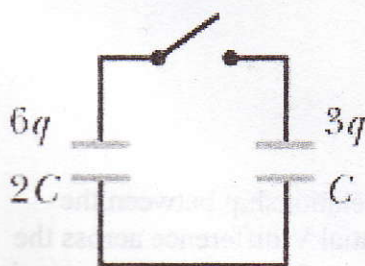
### Question 2


The figure below shows three circuits, each consisting of a switch and two capacitors, initially charged as indicated. After the switches have been closed, in which circuit (if any) will the charge on the left-hand capacitor (a) increase, (b) decrease, and (c) remain the same?



(1)

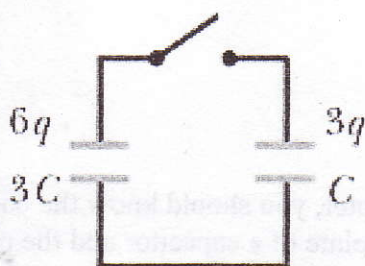

(2)

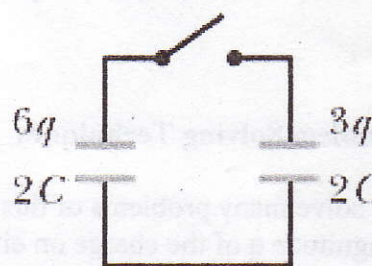

(3)

$\Rightarrow$  capacitors are in parallel so  $V$  must be the same  
 $(q = CV \rightarrow V = q/C \text{ must be the same for each})$

(a) circuit 2


(b) circuit 3

(c) circuit 1



### Question 3

Figure a shows a circuit with three capacitors, and Fig. b shows the circuit with their equivalent capacitor, of capacitance  $C_{eq}$ , which has a charge of  $60 \mu\text{C}$ . Without a calculator (and, if possible, without written calculation), find (a) the charge on and (b) the voltage across capacitor 3 and then (c) the charge on and (d) the voltage across capacitor 1.

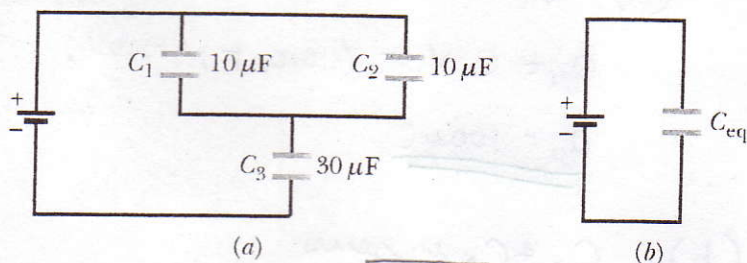

$$q_{12} = q_3 = 60 \mu\text{C}$$

$$(a) \quad q_3 = 60 \mu\text{C}$$

$$(b) \quad V_3 = q_3 / C_3 = \frac{60 \mu\text{C}}{30 \mu\text{F}} = 2 \text{ V}$$

$$(d) \quad V_{12} = q_{12} / C_{12} = \frac{60 \mu\text{C}}{20 \mu\text{F}} = 3 \text{ V} = V_1 = V_2$$

$$(c) \quad q_1 = C_1 V_1 = (10 \mu\text{F})(3 \text{ V}) = 30 \mu\text{C}$$

### Problem 1

A parallel-plate capacitor has circular plates of  $8.20 \text{ cm}$  radius and  $1.30 \text{ mm}$  separation. (a) Calculate the capacitance. (b) Find the charge for a potential difference of  $120 \text{ V}$ .

$$r = 8.20 \text{ cm} = 8.20 \times 10^{-2} \text{ m}$$

$$A = \pi r^2 = \pi (8.20 \times 10^{-2} \text{ m})^2 = 2.01 \times 10^{-2} \text{ m}^2$$

$$d = 1.30 \times 10^{-3} \text{ m}$$

$$(a) \quad C = \epsilon_0 A / d$$


$$C = \frac{(8.854 \times 10^{-12} \text{ C}^2/\text{Nm}^2)(2.01 \times 10^{-2} \text{ m}^2)}{(1.30 \times 10^{-3} \text{ m})}$$

$$C = 1.44 \times 10^{-10} \text{ F} = 14.4 \text{ nF}$$

$$(b) \quad q = CV = (1.44 \times 10^{-10} \text{ F})(120 \text{ V}) = 1.73 \times 10^{-8} \text{ C}$$
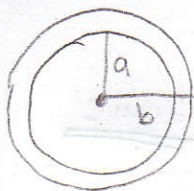
### Problem 2

Suppose that the two spherical shells of a spherical capacitor have approximately equal radii. Under these conditions, the device approximates a parallel-plate capacitor with  $b - a = d$ . Show that Eq. 25-17 ( $C = 4\pi\epsilon_0 ab / (b - a)$ ) does indeed reduce to Eq. 25-9 ( $C = \epsilon_0 A / d$ ) in this case.



$$\text{area of inner sphere} = 4\pi a^2$$

$$\text{area of outer sphere} = 4\pi b^2$$

since  $a \approx b$ , the area of either sphere can be written as

$$A \approx 4\pi ab$$

$$C = \frac{4\pi\epsilon_0 ab}{b-a} = \frac{\epsilon_0 (4\pi ab)}{b-a}$$


$$\begin{aligned} 4\pi ab &= A \\ b-a &= d \end{aligned}$$

$$C = \epsilon_0 A / d$$


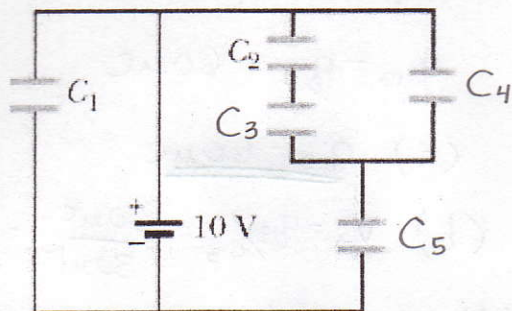
### Problem 3

In the figure below, the battery has a potential difference of 10.0 V and the five capacitors each have a capacitance of 10.0  $\mu\text{F}$ . What is the charge on (a) capacitor 1 and (b) capacitor 2?



(a)  $V_1 = 10\text{V}$


$$Q_1 = C_1 V_1 = (10.0\mu\text{F})(10.0\text{V})$$

$$\underline{Q_1 = 100\mu\text{C}}$$

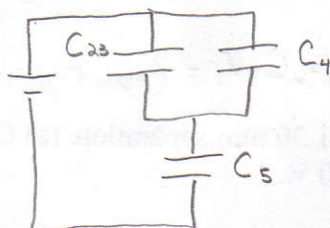(b)  $C_2 + C_3$  in series


$$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{10\mu\text{F}} + \frac{1}{10\mu\text{F}} = \frac{1}{5\mu\text{F}}$$

$$\frac{1}{C_{23}} = 0.20\mu\text{F}^{-1} \rightarrow C_{23} = 5\mu\text{F}$$




$$C_{23} + C_4 \text{ in parallel} \rightarrow C_{234} = C_{23} + C_4 = 5\mu\text{F} + 10\mu\text{F}$$

$$C_{234} = 15\mu\text{F}$$

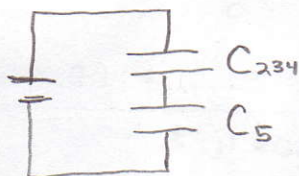

$$C_{234} + C_5 \text{ in series} \rightarrow \frac{1}{C_{2345}} = \frac{1}{C_{234}} + \frac{1}{C_5}$$
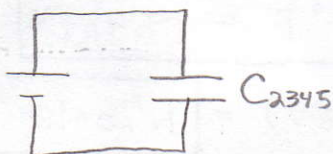
$$\frac{1}{C_{2345}} = \frac{1}{15\mu\text{F}} + \frac{1}{10\mu\text{F}} \rightarrow C_{2345} = 6\mu\text{F}$$



$$Q_{2345} = C_{2345} V_{2345} = (6\mu\text{F})(10\text{V}) = 60\mu\text{C} \rightarrow Q_{234} = Q_5 = 60\mu\text{C}$$

$$V_{234} = Q_{234} / C_{234} = \frac{60\mu\text{C}}{15\mu\text{F}} = 4\text{V} \rightarrow V_{23} = V_4 = 4\text{V} \quad (Q_4 = C_4 V_4 = 40\mu\text{C})$$

$$Q_{23} = C_{23} V_{23} = (5\mu\text{F})(4.0\text{V}) = 20\mu\text{C} \rightarrow Q_2 = Q_3 = \underline{20\mu\text{C}}$$

$$V_5 = Q_5 / C_5 = \frac{60\mu\text{C}}{10\mu\text{F}} = 6\text{V}$$

$$V_2 = Q_2 / C_2 = 20\mu\text{C} / 10\mu\text{F} = 2\text{V}$$

$$V_3 = Q_3 / C_3 = 20\mu\text{C} / 10\mu\text{F} = 2\text{V}$$

	Q	V
$C_1$	<u>100<math>\mu\text{C}</math></u>	10V
$C_2$	<u>20<math>\mu\text{C}</math></u>	2V
$C_3$	20 $\mu\text{C}$	2V
$C_4$	40 $\mu\text{C}$	4V
$C_5$	60 $\mu\text{C}$	6V



**Problem 4**

A 100 pF capacitor is charged to a potential difference of 50 V, and the charging battery is disconnected. The capacitor is then connected in parallel with a second (initially uncharged) capacitor. If the potential difference across the first capacitor drops to 35 V, what is the capacitance of this second capacitor?

$$\left. \begin{array}{l} C_1 = 100 \text{ pF} \\ V_0 = 50 \text{ V} \end{array} \right\} \text{ initially, the first capacitor has charge } q = C_1 V_0$$


$\Rightarrow$  after the first capacitor is connected in parallel to a second capacitor, its voltage drops to 35 V and it now has charge  $q_1 = C_1 V$

$\downarrow$  since charge is conserved, the second capacitor must have charge  $q_2 = q - q_1 = C_1 V_0 - C_1 V = C_1 (V_0 - V)$ ; its voltage is also 35 V since the capacitors are in parallel

$$C_2 = q_2 / V = C_1 (V_0 - V) / V = \frac{(100 \text{ pF})(50 \text{ V} - 35 \text{ V})}{35 \text{ V}} = \boxed{43 \text{ pF}}$$

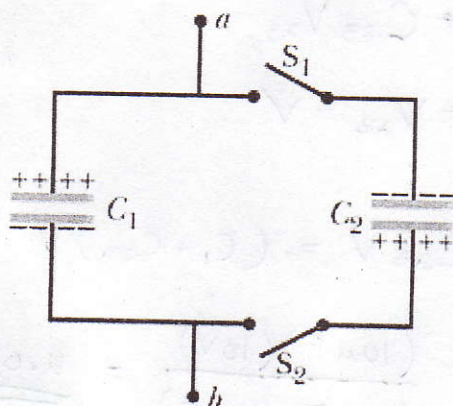**Problem 5**

In the figure below, the capacitances are  $C_1 = 1.0 \mu\text{F}$  and  $C_2 = 3.0 \mu\text{F}$  and both capacitors are charged to a potential difference of  $V = 100 \text{ V}$  but with opposite polarity as shown. Switches  $S_1$  and  $S_2$  are now closed. (a) What is now the potential difference between points a and b? What are now the charges on capacitors (b) 1 and (c) 2?



$\Rightarrow$  after the switch is closed, the capacitors are in parallel so the voltage across each is the same

$$\downarrow V_1 = V_2 = V_{12} = q_{12} / C_{12} \quad \begin{array}{l} q_{12} \rightarrow \text{total charge} \\ C_{12} \rightarrow C_{eq} \end{array}$$

$$q_1 = C_1 V_1 = (1.0 \mu\text{F})(100 \text{ V}) = 100 \mu\text{C}$$

$$q_2 = C_2 V_2 = (3.0 \mu\text{F})(100 \text{ V}) = 300 \mu\text{C}$$

\*  $q_{12} = 200 \mu\text{C}$  and not  $400 \mu\text{C}$  because the polarity is opposite

$$C_1 + C_2 \text{ are in parallel} \rightarrow C_{12} = C_1 + C_2 = 1.0 \mu\text{F} + 3.0 \mu\text{F} = 4.0 \mu\text{F}$$

$$V_{12} = q_{12} / C_{12} = \frac{200 \mu\text{C}}{4.0 \mu\text{F}} = \boxed{50 \text{ V}}$$

$$V_1 = V_2 = 50 \text{ V}$$


$$(b) \quad q_1 = C_1 V_1 = (1.0 \mu\text{F})(50 \text{ V}) = \boxed{50 \mu\text{C}}$$

$$q_2 = C_2 V_2 = (3.0 \mu\text{F})(50 \text{ V}) = \boxed{150 \mu\text{C}}$$



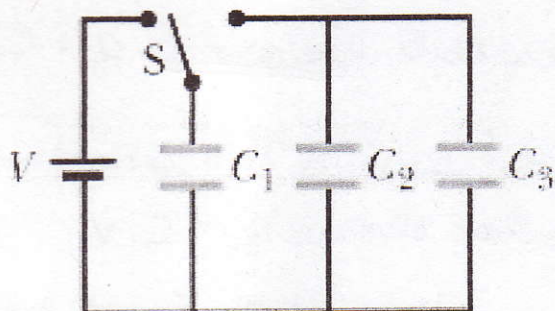
**Problem 6**

In the figure below,  $V = 10\text{ V}$ ,  $C_1 = 10\text{ }\mu\text{F}$ , and  $C_2 = C_3 = 20\text{ }\mu\text{F}$ . Switch  $S$  is first thrown to the left side until capacitor 1 reaches equilibrium. Then the switch is thrown to the right. When equilibrium is again reached, how much charge is on capacitor 1.



switch to left:

initial charge on  $C_1$

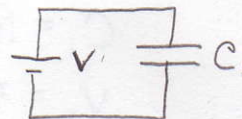

$$q = C_1 V_0 = (10\text{ }\mu\text{F})(10\text{ V}) = \underline{100\text{ }\mu\text{C}}$$

$C_2$  &  $C_3$  are in parallel  $\rightarrow C_{23} = C_2 + C_3 = 20\text{ }\mu\text{F} + 20\text{ }\mu\text{F}$

$$C_{23} = \underline{40\text{ }\mu\text{F}}$$

switch to right:

charge is conserved:  $q = q_1 + q_{23}$



$$C_1 V_0 = C_1 V_1 + C_{23} V_{23}$$

$$\downarrow V_1 = V_{23} = V$$

$$C_1 V_0 = C_1 V + C_{23} V = (C_1 + C_{23}) V$$

$$V = \frac{C_1 V_0}{(C_1 + C_{23})} = \frac{(10\text{ }\mu\text{F})(10\text{ V})}{(10\text{ }\mu\text{F} + 40\text{ }\mu\text{F})} = \underline{2.0\text{ V}}$$

$$V_1 = 2.0\text{ V}$$

$$V_{23} = 2.0\text{ V}$$

$$q_1 = C_1 V_1 = (10\text{ }\mu\text{F})(2.0\text{ V}) = \boxed{20\text{ }\mu\text{C}}$$

$$q_{23} = C_{23} V_{23} = (40\text{ }\mu\text{F})(2.0\text{ V}) = 80\text{ }\mu\text{C}$$



**Problem 7**

The parallel-plates in a capacitor, with a plate area of  $8.50 \text{ cm}^2$  and an air-filled separation of  $3.00 \text{ mm}$ , are charged by a  $6.00 \text{ V}$  battery. They are then disconnected from the battery and pulled apart (without discharge) to a separation of  $8.00 \text{ mm}$ . Neglecting fringing, find (a) the potential difference between the plates (b) the initial stored energy, (c) the final stored energy and (d) the work required to separate the plates.

$$A = 8.50 \text{ cm}^2 = 8.50 \times 10^{-4} \text{ m}^2$$

$$d = 3.00 \text{ mm} = 3.00 \times 10^{-3} \text{ m}$$

$$V = 6.00 \text{ V}$$

$C = \epsilon_0 A/d$  once capacitor is disconnected from the battery, the charge remains the same

$$\text{originally} \rightarrow C = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2)(8.50 \times 10^{-4} \text{ m}^2)}{(3.00 \times 10^{-3} \text{ m})}$$

$$C = 2.51 \times 10^{-12} \text{ F} \quad V = 6.00 \text{ V} \quad q = CV = (2.51 \times 10^{-12} \text{ F})(6.00 \text{ V}) = 1.51 \times 10^{-11} \text{ C}$$

now charge remains same

$$C = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2)(8.50 \times 10^{-4} \text{ m}^2)}{(8.00 \times 10^{-3} \text{ m})} = 9.40 \times 10^{-13} \text{ F}$$

$$(a) V = q/C = \frac{1.51 \times 10^{-11} \text{ C}}{9.40 \times 10^{-13} \text{ F}}$$

$$V = 16 \text{ V}$$

$$(b) U = \frac{1}{2} C_i V_i^2 = \frac{1}{2} (2.51 \times 10^{-12} \text{ F})(6.00 \text{ V})^2 = 4.51 \times 10^{-11} \text{ J}$$

$$(c) U = \frac{1}{2} C_f V_f^2 = 1.20 \times 10^{-10} \text{ J}$$

$$(d) W = \Delta U \approx 7.52 \times 10^{-11} \text{ J}$$

**Problem 8**

A parallel-plate air-filled capacitor has a capacitance of  $50 \text{ pF}$ . (a) If each of its plates has an area of  $0.35 \text{ m}^2$ , what is the separation? (b) If the region between the plates is now filled with material having  $\kappa = 5.6$ , what is the capacitance?

$$C = 50 \text{ pF}$$

$$A = 0.35 \text{ m}^2$$

$$\kappa = 5.6$$

$$(a) C = \epsilon_0 A/d \rightarrow d = \epsilon_0 A/C$$

$$d = \frac{(8.85 \times 10^{-12} \text{ F/m})(0.35 \text{ m}^2)}{(50 \times 10^{-12} \text{ F})}$$

$$d = 6.2 \times 10^{-3} \text{ m}$$

(b) with a dielectric between the plates, the new capacitance is given by:

$$C_{\text{new}} = (\kappa \epsilon_0) A/d = \kappa (\epsilon_0 A/d) = \kappa C_{\text{old}}$$

$$C_{\text{new}} = (5.6)(50 \text{ pF}) = 280 \text{ pF}$$



**Problem 9**

The space between two concentric conducting spherical shells of radii  $a = 1.70$  cm and  $b = 1.20$  cm is filled with a substance of dielectric constant  $\kappa = 23.5$ . A potential difference  $V = 73.0$  V is applied across the inner and outer shells. Determine (a) the capacitance of the device, (b) the free charge  $q$  on the inner shell, and (c) the charge  $q'$  induced along the surface of the inner shell.


$$\begin{aligned}
 a &= 1.70 \times 10^{-2} \text{ m} \\
 b &= 1.20 \times 10^{-2} \text{ m} \\
 K &= 23.5 \\
 V &= 73.0 \text{ V}
 \end{aligned}
 \quad
 \begin{aligned}
 (a) \quad C_0 &= 4\pi\epsilon_0 \left( \frac{ab}{a-b} \right) \rightarrow C = KC_0 = 4\pi K\epsilon_0 \left( \frac{ab}{a-b} \right) \\
 C &= 4\pi(23.5)(8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2) \left[ \frac{(1.70 \times 10^{-2} \text{ m})(1.20 \times 10^{-2} \text{ m})}{0.50 \times 10^{-2} \text{ m}} \right] \\
 C &= 1.07 \times 10^{-8} \text{ F} = \boxed{0.107 \text{ nF}}
 \end{aligned}$$

$$(b) \text{ free charge } q = CV = (1.07 \times 10^{-8} \text{ F})(73.0 \text{ V}) = \boxed{7.79 \text{ nC}}$$

$$\begin{aligned}
 (c) \quad q - q' &= q/K \rightarrow q' = q - q/K = q(1 - 1/K) \\
 q' &= (7.79 \text{ nC}) \left( 1 - \frac{1}{23.5} \right) = \boxed{7.46 \text{ nC}}
 \end{aligned}$$

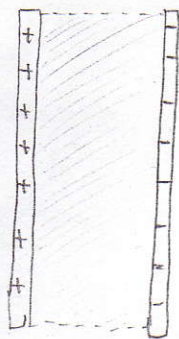**Problem 10**

Two parallel plates of area  $100 \text{ cm}^2$  are given charges of equal magnitudes  $8.9 \times 10^{-7} \text{ C}$  but opposite signs. The electric field within the dielectric material filling the space between the plates is  $1.4 \times 10^6 \text{ V/m}$ . (a) Calculate the dielectric constant of the material. (b) Determine the magnitude of the charge induced on each dielectric surface.



$$\begin{aligned}
 q &= 8.9 \times 10^{-7} \text{ C} \\
 E &= 1.4 \times 10^6 \text{ V/m} \\
 A &= 100 \text{ cm}^2 \left( \frac{1 \text{ m}}{100 \text{ cm}} \right)^2 = 10^{-2} \text{ m}^2 \\
 \text{with a dielectric, } E &= E_0/K = \frac{q}{K\epsilon_0 A}
 \end{aligned}$$

$$\begin{aligned}
 (a) \quad K &= \frac{q}{\epsilon_0 EA} \rightarrow K = \frac{(8.9 \times 10^{-7} \text{ C})}{(8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2)(1.4 \times 10^6 \text{ V/m})(10^{-2} \text{ m}^2)} \\
 K &= \boxed{7.2}
 \end{aligned}$$

$$\begin{aligned}
 (b) \quad q - q' &= q/K \quad \text{where } q' = \text{induced charge} \\
 &\quad q = \text{charge on plates}
 \end{aligned}$$

$$\begin{aligned}
 q' &= q - q/K = q(1 - 1/K) \\
 &= (8.9 \times 10^{-7} \text{ C}) \left( 1 - \frac{1}{7.2} \right) \rightarrow \boxed{q' = 7.7 \times 10^{-7} \text{ C}}
 \end{aligned}$$