

$$\text{ave.} = 7.6$$

$$\sigma = 2.5$$

Name: Answer Key

Lab (circle one): 8:00 am 11:15 am 2:45 pm




Quiz #6: Circuits

Problem 1 (2 points)

The equivalent resistance between points a and b in the circuit shown to the right is:

- a) 6.0 Ω
b) 7.2 Ω
c) 8.0 Ω
d) 9.0 Ω
e) none of the above

A

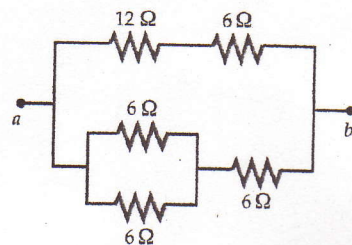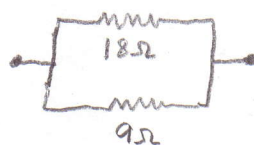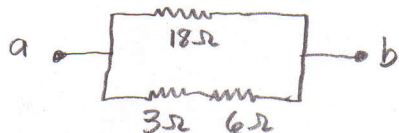

Problem 2 (3 points)


Use Kirchoff's rules to write three independent equations for the circuit shown to the right.

from junction rule: $i_1 + i_2 = i_3$

from left loop: $E_1 - i_1 R_1 - i_3 R_2 - E_2 - i_1 R_1 = 0$


$$E_1 - E_2 - 2i_1 R_1 - i_3 R_2 = 0$$

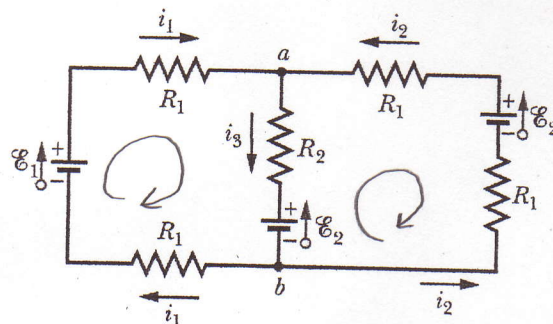from right loop: $E_2 + i_3 R_2 + i_2 R_1 - E_2 + i_2 R_1 = 0 \rightarrow 2i_2 R_1 + i_3 R_2 = 0$



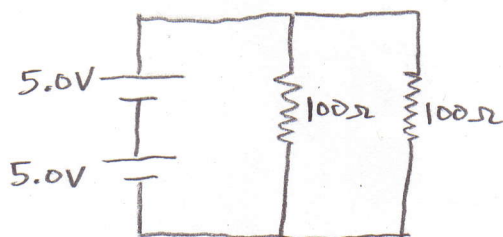Problem 3 (2 points)

You have two identical 100 Ω resistors and two identical ideal 5.0 V batteries. Draw a circuit diagram of how you would arrange the resistors and batteries in order to get the maximum possible total power out of the resistors.




for a resistor, $P = iV = i^2 R$

to maximize P we want to maximize the current through each resistor

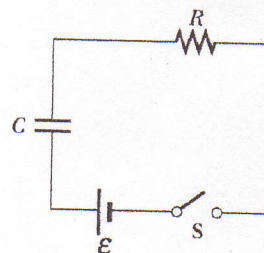Problem 4 (3 points)

In the circuit to the right, $R = 750 \Omega$ and the capacitor is initially uncharged. The switch is then closed, and after 0.015 s, the charge on the capacitor has increased to half of its final value. What is the capacitance of the capacitor?



for charging a capacitor: $q = q_0(1 - e^{-t/\tau})$ $\tau = RC$

$q = \frac{1}{2}q_0$ at $t = 0.015$ s

$$\frac{1}{2}q_0 = q_0(1 - e^{-t/\tau}) \rightarrow \frac{1}{2} = 1 - e^{-t/\tau} \rightarrow e^{-t/\tau} = \frac{1}{2}$$

$$-t/\tau = \ln(1/2) \rightarrow \tau = \frac{-t}{\ln(1/2)} = \frac{-0.015}{\ln(1/2)} \rightarrow \tau = 0.0216$$

$$\tau = RC \rightarrow C = \frac{\tau}{R} = \frac{0.0216}{750} = 28.9 \mu F$$