

ave. = 6.5
 $\sigma = 2.3$

Name: _____

Answer Key

Lab (circle one): 8:00 am 11:15 am 2:30 pm

Quiz #6: Circuits

Problem 1 (1 point)


The figure below shows three sections of a circuit that are to be connected to a battery. The resistors are identical, as are the capacitors. Rank the sections according to the time required to reach 50% of its final charge, greatest first.

- a) all tie
b) 1, 2 and 3 tie
c) 2 and 3 tie, 1
d) 1, 3, 2
e) 2, 3, 1
f) none of the above




(1)

$\tau = (2R)C$

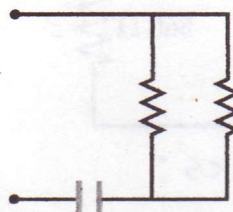

(2)

$\tau = (R/2)C$

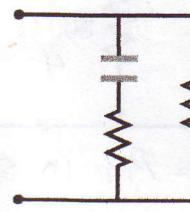

(3)


$\tau = RC$

note: resistors are not in parallel

Problem 2 (1 point)


A portion of a circuit is shown, with the values of the currents given for some branches. What is the direction and value of the current i ?

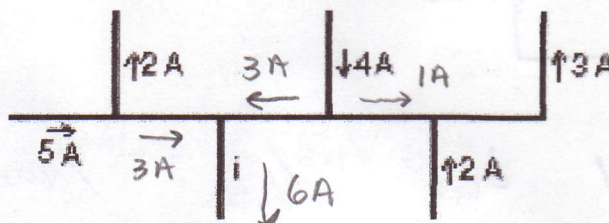- a) \downarrow , 6A
b) \uparrow , 6A
c) \downarrow , 4A
d) \uparrow , 4A
e) \downarrow , 2A
f) none of the above



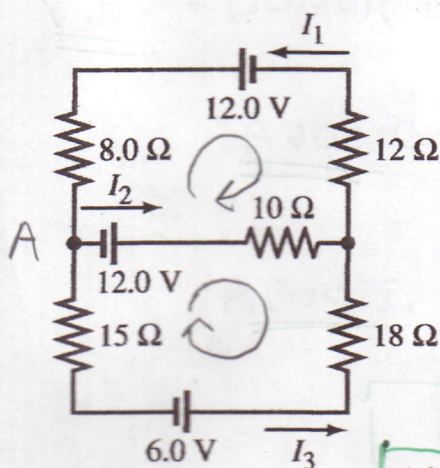Problem 3 (3 points)

Use Kirchhoff's rules to write three independent equations for the circuit shown below. (Note: you do not have to solve the equations.)



junction rule:

$I_1 = I_2 + I_3$

all loops start at A and go CW:

top loop:

$I_1(8.0\Omega) - 12.0V + I_1(12\Omega) + I_2(10\Omega) - 12V = 0$

bottom loop:


$12V - I_2(10\Omega) + I_3(18\Omega) - 6.0V + I_3(15\Omega) = 0$

outside loop:

$I_1(8.0\Omega) - 12.0V + I_1(12\Omega) + I_3(18\Omega) - 6.0V + I_3(15\Omega) = 0$

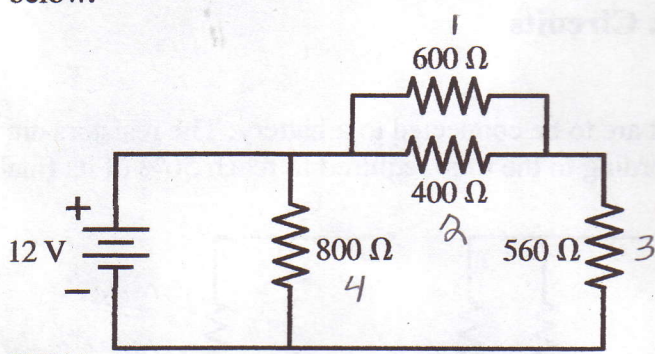Problem 4 (5 points)

Find the current through and the potential difference across each of the four resistors shown in the figure below.




$R_1 + R_2$ in parallel:

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{600\Omega} + \frac{1}{400\Omega}$$

$$R_{12} = \underline{240\Omega}$$

$R_{12} + R_3$ in series:
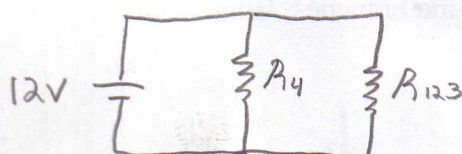
$$R_{123} = R_{12} + R_3 = 240\Omega + 560\Omega = \underline{800\Omega}$$



$$V_4 = 12V \quad i_4 = V_4/R_4 = 12V/800\Omega = \underline{0.015A}$$

$$V_{123} = 12V \quad i_{123} = V_{123}/R_{123} = 12V/800\Omega = \underline{0.015A}$$

$$i_3 = i_{123} = \underline{0.015A} \quad V_3 = i_3 R_3 = (0.015A)(560\Omega) = \underline{8.4V}$$

$$i_{12} = i_{123} = \underline{0.015A} \quad V_{12} = i_{12} R_{12} = (0.015A)(240\Omega) = \underline{3.6V}$$

$$V_1 = V_{12} = \underline{3.6V} \quad i_1 = V_1/R_1 = \frac{3.6V}{600\Omega} = \underline{0.006A}$$

$$V_2 = V_{12} = \underline{3.6V} \quad i_2 = V_2/R_2 = \frac{3.6V}{400\Omega} = \underline{0.009A}$$

$$600\Omega \quad V = 3.6V \quad i = 0.006A$$

$$400\Omega \quad V = 3.6V \quad i = 0.009A$$

$$560\Omega \quad V = 8.4V \quad i = 0.015A$$

$$800\Omega \quad V = 12V \quad i = 0.015A$$