

# Physics 4B

## Solutions to Chapter 27 HW

Chapter 27: Questions: 2, 8, 10  
Problems: 1, 23, 33, 45, 48, 61, 63, 72, 92

---

### Question 27-2

(a) no (b) yes (c) all tie

### Question 27-8

$60 \mu\text{C}$

### Question 27-10

1, *c*; 2, *a*; 3, *d*; 4, *b*

### Problem 27-1

(a) Let  $i$  be the current in the circuit and take it to be positive if it is to the left in  $R_1$ . We use Kirchhoff's loop rule:  $\varepsilon_1 - iR_2 - iR_1 - \varepsilon_2 = 0$ . We solve for  $i$ :

$$i = \frac{\varepsilon_1 - \varepsilon_2}{R_1 + R_2} = \frac{12 \text{ V} - 6.0 \text{ V}}{4.0 \Omega + 8.0 \Omega} = 0.50 \text{ A}.$$

A positive value is obtained, so the current is counterclockwise around the circuit.

If  $i$  is the current in a resistor  $R$ , then the power dissipated by that resistor is given by  $P = i^2 R$ .

(b) For  $R_1$ ,  $P_1 = i^2 R_1 = (0.50 \text{ A})^2 (4.0 \Omega) = 1.0 \text{ W}$ ,

(c) and for  $R_2$ ,  $P_2 = i^2 R_2 = (0.50 \text{ A})^2 (8.0 \Omega) = 2.0 \text{ W}$ .

If  $i$  is the current in a battery with emf  $\varepsilon$ , then the battery supplies energy at the rate  $P = i\varepsilon$  provided the current and emf are in the same direction. The battery absorbs energy at the rate  $P = i\varepsilon$  if the current and emf are in opposite directions.

(d) For  $\varepsilon_1$ ,  $P_1 = i\varepsilon_1 = (0.50 \text{ A})(12 \text{ V}) = 6.0 \text{ W}$

(e) and for  $\varepsilon_2$ ,  $P_2 = i\varepsilon_2 = (0.50 \text{ A})(6.0 \text{ V}) = 3.0 \text{ W}$ .

(f) In battery 1 the current is in the same direction as the emf. Therefore, this battery supplies energy to the circuit; the battery is discharging.

(g) The current in battery 2 is opposite the direction of the emf, so this battery absorbs energy from the circuit. It is charging.

### Problem 27-23

Let  $i_1$  be the current in  $R_1$  and take it to be positive if it is to the right. Let  $i_2$  be the current in  $R_2$  and take it to be positive if it is upward.

(a) When the loop rule is applied to the lower loop, the result is

$$\varepsilon_2 - i_1 R_1 = 0.$$

The equation yields

$$i_1 = \frac{\varepsilon_2}{R_1} = \frac{5.0 \text{ V}}{100 \Omega} = 0.050 \text{ A}.$$

(b) When it is applied to the upper loop, the result is

$$\varepsilon_1 - \varepsilon_2 - \varepsilon_3 - i_2 R_2 = 0.$$

The equation gives

$$i_2 = \frac{\varepsilon_1 - \varepsilon_2 - \varepsilon_3}{R_2} = \frac{6.0 \text{ V} - 5.0 \text{ V} - 4.0 \text{ V}}{50 \Omega} = -0.060 \text{ A},$$

or  $|i_2| = 0.060 \text{ A}$ . The negative sign indicates that the current in  $R_2$  is actually downward.

(c) If  $V_b$  is the potential at point  $b$ , then the potential at point  $a$  is  $V_a = V_b + \varepsilon_3 + \varepsilon_2$ , so

$$V_a - V_b = \varepsilon_3 + \varepsilon_2 = 4.0 \text{ V} + 5.0 \text{ V} = 9.0 \text{ V}.$$

### Problem 27-33

First, we note in  $V_4$ , that the voltage across  $R_4$  is equal to the sum of the voltages across  $R_5$  and  $R_6$ :

$$V_4 = i_6(R_5 + R_6) = (1.40 \text{ A})(8.00 \Omega + 4.00 \Omega) = 16.8 \text{ V}.$$

The current through  $R_4$  is then equal to  $i_4 = V_4/R_4 = 16.8 \text{ V}/(16.0 \Omega) = 1.05 \text{ A}$ .

By the junction rule, the current in  $R_2$  is

$$i_2 = i_4 + i_6 = 1.05 \text{ A} + 1.40 \text{ A} = 2.45 \text{ A},$$

so its voltage is  $V_2 = (2.00 \Omega)(2.45 \text{ A}) = 4.90 \text{ V}$ .

The loop rule tells us the voltage across  $R_3$  is  $V_3 = V_2 + V_4 = 21.7 \text{ V}$  (implying that the current through it is  $i_3 = V_3/(2.00 \Omega) = 10.85 \text{ A}$ ).

The junction rule now gives the current in  $R_1$  as  $i_1 = i_2 + i_3 = 2.45 \text{ A} + 10.85 \text{ A} = 13.3 \text{ A}$ , implying that the voltage across it is  $V_1 = (13.3 \text{ A})(2.00 \Omega) = 26.6 \text{ V}$ . Therefore, by the loop rule,

$$\varepsilon = V_1 + V_3 = 26.6 \text{ V} + 21.7 \text{ V} = 48.3 \text{ V}.$$

### Problem 27-45

(a) We note that the  $R_1$  resistors occur in series pairs, contributing net resistance  $2R_1$  in each branch where they appear. Since  $\varepsilon_2 = \varepsilon_3$  and  $R_2 = 2R_1$ , from symmetry we know that the currents through  $\varepsilon_2$  and  $\varepsilon_3$  are the same:  $i_2 = i_3 = i$ . Therefore, the current through  $\varepsilon_1$  is  $i_1 = 2i$ . Then from  $V_b - V_a = \varepsilon_2 - iR_2 = \varepsilon_1 + (2R_1)(2i)$  we get

$$i = \frac{\varepsilon_2 - \varepsilon_1}{4R_1 + R_2} = \frac{4.0 \text{ V} - 2.0 \text{ V}}{4(1.0 \Omega) + 2.0 \Omega} = 0.33 \text{ A}.$$

Therefore, the current through  $\varepsilon_1$  is  $i_1 = 2i = 0.67 \text{ A}$ .

(b) The direction of  $i_1$  is downward.

(c) The current through  $\varepsilon_2$  is  $i_2 = 0.33 \text{ A}$ .

(d) The direction of  $i_2$  is upward.

(e) From part (a), we have  $i_3 = i_2 = 0.33 \text{ A}$ .

(f) The direction of  $i_3$  is also upward.

(g)  $V_a - V_b = -iR_2 + \varepsilon_2 = -(0.333 \text{ A})(2.0 \Omega) + 4.0 \text{ V} = 3.3 \text{ V}$ .

### Problem 27-48

(a) We use  $P = \varepsilon^2/R_{\text{eq}}$ , where

$$R_{\text{eq}} = 7.00 \Omega + \frac{(12.0 \Omega)(4.00 \Omega)R}{(12.0 \Omega)(4.0 \Omega) + (12.0 \Omega)R + (4.00 \Omega)R}.$$

Put  $P = 60.0 \text{ W}$  and  $\varepsilon = 24.0 \text{ V}$  and solve for  $R$ :  $R = 19.5 \Omega$ .

(b) Since  $P \propto R_{\text{eq}}$ , we must minimize  $R_{\text{eq}}$ , which means  $R = 0$ .

(c) Now we must maximize  $R_{\text{eq}}$ , or set  $R = \infty$ .

(d) Since  $R_{\text{eq, min}} = 7.00 \Omega$ ,  $P_{\text{max}} = \varepsilon^2/R_{\text{eq, min}} = (24.0 \text{ V})^2/7.00 \Omega = 82.3 \text{ W}$ .

(e) Since  $R_{\text{eq, max}} = 7.00 \Omega + (12.0 \Omega)(4.00 \Omega)/(12.0 \Omega + 4.00 \Omega) = 10.0 \Omega$ ,

$$P_{\text{min}} = \varepsilon^2/R_{\text{eq, max}} = (24.0 \text{ V})^2/10.0 \Omega = 57.6 \text{ W}.$$

**Problem 27-61**

(a) The voltage difference  $V$  across the capacitor is  $V(t) = \mathcal{E}(1 - e^{-t/RC})$ . At  $t = 1.30 \mu\text{s}$  we have  $V(t) = 5.00 \text{ V}$ , so  $5.00 \text{ V} = (12.0 \text{ V})(1 - e^{-1.30 \mu\text{s}/RC})$ , which gives

$$\tau = (1.30 \mu\text{s})/\ln(12/7) = 2.41 \mu\text{s}.$$

(b) The capacitance is  $C = \tau/R = (2.41 \mu\text{s})/(15.0 \text{ k}\Omega) = 161 \text{ pF}$ .

**Problem 27-63**

At  $t = 0$  the capacitor is completely uncharged and the current in the capacitor branch is as it would be if the capacitor were replaced by a wire. Let  $i_1$  be the current in  $R_1$  and take it to be positive if it is to the right. Let  $i_2$  be the current in  $R_2$  and take it to be positive if it is downward. Let  $i_3$  be the current in  $R_3$  and take it to be positive if it is downward. The junction rule produces  $i_1 = i_2 + i_3$ , the loop rule applied to the left-hand loop produces

$$\mathcal{E} - i_1 R_1 - i_2 R_2 = 0,$$

and the loop rule applied to the right-hand loop produces

$$i_2 R_2 - i_3 R_3 = 0.$$

Since the resistances are all the same we can simplify the mathematics by replacing  $R_1$ ,  $R_2$ , and  $R_3$  with  $R$ .

(a) Solving the three simultaneous equations, we find

$$i_1 = \frac{2\mathcal{E}}{3R} = \frac{2(1.2 \times 10^3 \text{ V})}{3(0.73 \times 10^6 \Omega)} = 1.1 \times 10^{-3} \text{ A},$$

(b)  $i_2 = \frac{\mathcal{E}}{3R} = \frac{1.2 \times 10^3 \text{ V}}{3(0.73 \times 10^6 \Omega)} = 5.5 \times 10^{-4} \text{ A}$ , and

(c)  $i_3 = i_2 = 5.5 \times 10^{-4} \text{ A}$ .

At  $t = \infty$  the capacitor is fully charged and the current in the capacitor branch is 0. Thus,  $i_1 = i_2$ , and the loop rule yields

$$\mathcal{E} - i_1 R_1 - i_1 R_2 = 0.$$

(d) The solution is

$$i_1 = \frac{\mathcal{E}}{2R} = \frac{1.2 \times 10^3 \text{ V}}{2(0.73 \times 10^6 \Omega)} = 8.2 \times 10^{-4} \text{ A}.$$

(e)  $i_2 = i_1 = 8.2 \times 10^{-4} \text{ A}$ .

(f) As stated before, the current in the capacitor branch is  $i_3 = 0$ .

We take the upper plate of the capacitor to be positive. This is consistent with current flowing into that plate. The junction equation is  $i_1 = i_2 + i_3$ , and the loop equations are

$$\begin{aligned}\varepsilon - i_1 R - i_2 R &= 0 \\ -\frac{q}{C} - i_3 R + i_2 R &= 0.\end{aligned}$$

We use the first equation to substitute for  $i_1$  in the second and obtain  $\varepsilon - 2i_2 R - i_3 R = 0$ . Thus  $i_2 = (\varepsilon - i_3 R)/2R$ . We substitute this expression into the third equation above to obtain

$$-(q/C) - (i_3 R) + (\varepsilon/2) - (i_3 R/2) = 0.$$

Now we replace  $i_3$  with  $dq/dt$  to obtain

$$\frac{3R}{2} \frac{dq}{dt} + \frac{q}{C} = \frac{\varepsilon}{2}.$$

This is just like the equation for an  $RC$  series circuit, except that the time constant is  $\tau = 3RC/2$  and the impressed potential difference is  $\varepsilon/2$ . The solution is

$$q = \frac{C\varepsilon}{2} (1 - e^{-2t/3RC}).$$

The current in the capacitor branch is

$$i_3(t) = \frac{dq}{dt} = \frac{\varepsilon}{3R} e^{-2t/3RC}.$$

The current in the center branch is

$$i_2(t) = \frac{\varepsilon}{2R} - \frac{i_3}{2} = \frac{\varepsilon}{2R} - \frac{\varepsilon}{6R} e^{-2t/3RC} = \frac{\varepsilon}{6R} (3 - e^{-2t/3RC})$$


and the potential difference across  $R_2$  is

$$V_2(t) = i_2 R = \frac{\varepsilon}{6} (3 - e^{-2t/3RC}).$$

(g) For  $t = 0$ ,  $e^{-2t/3RC} = 1$  and  $V_2 = \varepsilon/3 = (1.2 \times 10^3 \text{ V})/3 = 4.0 \times 10^2 \text{ V}$ .

(h) For  $t = \infty$ ,  $e^{-2t/3RC} \rightarrow 0$  and  $V_2 = \varepsilon/2 = (1.2 \times 10^3 \text{ V})/2 = 6.0 \times 10^2 \text{ V}$ .

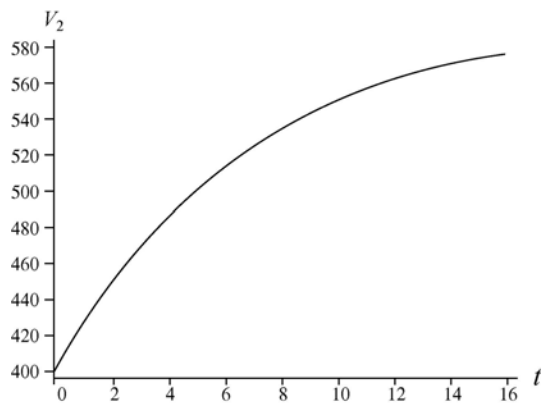(i) A plot of  $V_2$  as a function of time is shown in the following graph.



### Problem 27-72

(a) The four resistors  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$  on the left reduce to

$$R_{\text{eq}} = R_{12} + R_{34} = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4} = 7.0 \, \Omega + 3.0 \, \Omega = 10 \, \Omega.$$

With  $\mathcal{E} = 30 \, \text{V}$  across  $R_{\text{eq}}$  the current there is  $i_2 = 3.0 \, \text{A}$ .

(b) The three resistors on the right reduce to

$$R'_{\text{eq}} = R_{56} + R_7 = \frac{R_5 R_6}{R_5 + R_6} + R_7 = \frac{(6.0 \, \Omega)(2.0 \, \Omega)}{6.0 \, \Omega + 2.0 \, \Omega} + 1.5 \, \Omega = 3.0 \, \Omega.$$

With  $\mathcal{E} = 30 \, \text{V}$  across  $R'_{\text{eq}}$  the current there is  $i_4 = 10 \, \text{A}$ .

(c) By the junction rule,  $i_1 = i_2 + i_4 = 13 \, \text{A}$ .

(d) By symmetry,  $i_3 = \frac{1}{2} i_2 = 1.5 \, \text{A}$ .

(e) By the loop rule (proceeding clockwise),

$$30\text{V} - i_4(1.5 \, \Omega) - i_5(2.0 \, \Omega) = 0$$

readily yields  $i_5 = 7.5 \, \text{A}$ .

### Problem 27-92

The equivalent resistance of the series pair of  $R_3 = R_4 = 2.0 \, \Omega$  is  $R_{34} = 4.0 \, \Omega$ , and the equivalent resistance of the parallel pair of  $R_1 = R_2 = 4.0 \, \Omega$  is  $R_{12} = 2.0 \, \Omega$ . Since the voltage across  $R_{34}$  must equal that across  $R_{12}$ :

$$V_{34} = V_{12} \Rightarrow i_{34} R_{34} = i_{12} R_{12} \Rightarrow i_{34} = \frac{1}{2} i_{12}$$

This relation, plus the junction rule condition  $I = i_{12} + i_{34} = 6.00$  A, leads to the solution  $i_{12} = 4.0$  A . It is clear by symmetry that  $i_1 = i_{12} / 2 = 2.00$  A .