

Quiz #9: EM Oscillations and Alternating Current


Problem 1 (1 point)

An RLC series circuit is driven by a sinusoidal emf with angular frequency ω_d . If ω_d is increased without changing the amplitude of the emf, the current amplitude increases. This means that:

- a) $\omega_d L > R$
- b) $\omega_d L < R$
- c) $\omega_d L > 1/\omega_d C$
- d) $\omega_d L < 1/\omega_d C$
- e) $\omega_d L = 1/\omega_d C$

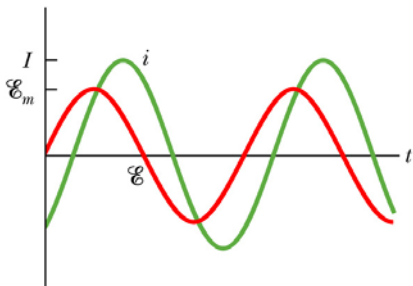Problem 2 (2 points)


The figure below shows the current i and driving emf ε for a series RLC circuit driven at frequency f_d . What effect (increase, decrease, or no change) would each of the following changes have on (a) the current amplitude I and (b) the phase angle ϕ ?



	Effect on I	Effect on ϕ
Increase L		
Increase R		
Increase C		
Increase f_d		

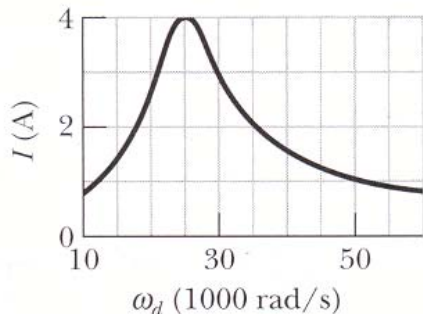Problem 3 (2 points)

The current amplitude I versus driving frequency ω_d for a series RLC circuit is given in the figure below (**Note:** the driving angular frequency is given in units of **1000** rad/s). The inductance is 175 μH and the emf amplitude is $\varepsilon_m = 125$ V. What are the values of (a) C and (b) R ?



Problem 4 (2 points)

In an oscillating LC circuit, $L = 30.0 \text{ mH}$ and $C = 7.50 \text{ }\mu\text{F}$. At time $t = 1.50 \text{ s}$, the current is 9.0 mA and the charge on the capacitor is $3.50 \text{ }\mu\text{C}$. **(a)** What is the maximum charge on the capacitor? **(b)** What is the maximum current?

Problem 5 (3 points)

In the figure below, let $R = 100.0 \Omega$, $C = 25.0 \text{ }\mu\text{F}$, $L = 200.0 \text{ mH}$, $f_d = 60.0 \text{ Hz}$, and $\xi_m = 30.0 \text{ V}$.

(a) What is the maximum current in the circuit? **(b)** What are the rms voltages across the resistor, capacitor, and the inductor?

