

Review Problems for the Final Exam

Problem 1

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t$$

$$i = I \sin(\omega_d t - \phi) \quad I = \mathcal{E}_m / Z = \mathcal{E}_m / \sqrt{R^2 + (X_L - X_C)^2} \quad \tan \phi = \frac{X_L - X_C}{R}$$

↓

from i we can get $V_R = iR$, $V_L = L di/dt$, $V_C = q/C$ $q = \int i dt$

⇒ need I and ϕ

$$X_L = 2\pi f_d L = 75.4 \Omega \quad X_C = \frac{1}{2\pi f_d C} = 106.1 \Omega \quad Z = 104.6 \Omega$$

$$I = \mathcal{E}_m / Z = \frac{30.0 \text{ V}}{104.6 \Omega} = 0.287 \text{ A} \quad \phi = \tan^{-1} \left(\frac{75.4 \Omega - 106.1 \Omega}{100 \Omega} \right) = -17.1^\circ$$

⇒ voltage across generator is a max (30.0 V) when $\sin \omega_d t = 1$
or $\omega_d t = \pi/2 = 90^\circ$

↓

short cut: don't solve for $t \rightarrow \omega_d t - \phi = 90^\circ - (-17.1^\circ) = 107.1^\circ$

resistor → $V_R = iR = IR \sin(\omega_d t - \phi)$

$$= (0.287 \text{ A})(100 \Omega) \sin(107.1^\circ)$$

$$V_R = 27.4 \text{ V}$$

inductor $\rightarrow V_L = L \frac{di}{dt} = L \frac{d}{dt} [I \sin(\omega_d t - \phi)]$
 $= L I \omega_d \cos(\omega_d t - \phi)$

$$V_L = (200 \times 10^{-3} \text{ H})(0.287 \text{ A}) 2\pi(60 \text{ Hz}) \cos(107.1^\circ)$$

$$V_L = -6.4 \text{ V}$$

capacitor $\rightarrow V_C = q/C \quad q = \int i dt = \int I \sin(\omega_d t - \phi)$
 $= -I/\omega_d \cos(\omega_d t - \phi)$

$$V_C = \frac{-I}{\omega_d C} \cos(\omega_d t - \phi)$$

$$V_C = \frac{-(0.287 \text{ A})}{2\pi(60 \text{ Hz})(25.0 \times 10^{-6} \text{ F})} \cos(107.1^\circ)$$

$$V_C = 9.6 \text{ V}$$

note: $V_R + V_L + V_C = \mathcal{E}$

Problem 2

$$V = \frac{\sigma}{2\epsilon_0} (\sqrt{z^2 + R^2} - z)$$

$$E_z = -\frac{\partial V}{\partial z} = -\frac{\sigma}{2\epsilon_0} \frac{\partial}{\partial z} [(\sqrt{z^2 + R^2}) - z]$$

$$E_z = -\frac{\sigma}{2\epsilon_0} \left[\frac{1}{2} (z^2 + R^2)^{-1/2} (2z) - 1 \right]$$

$$E_z = \frac{\sigma}{2\epsilon_0} \left[1 - \frac{z}{\sqrt{z^2 + R^2}} \right]$$

$$\text{for } R \gg z \rightarrow \frac{z}{\sqrt{z^2 + R^2}} \rightarrow 0 \quad E_z = \frac{\sigma}{2\epsilon_0} [1 - 0] = \sigma/2\epsilon_0$$

$$E = \sigma/2\epsilon_0 \rightarrow E \text{ from an infinite sheet}$$

$$\begin{aligned} \text{for } z \gg R \quad \frac{z}{\sqrt{z^2 + R^2}} &= z (z^2 + R^2)^{-1/2} = z (z^2)^{-1/2} (1 + R^2/z^2)^{-1/2} \\ &= z (z^{-1}) (1 + R^2/z^2)^{-1/2} = (1 + R^2/z^2)^{-1/2} \end{aligned}$$

$$\text{for } x \ll 1 \rightarrow (1+x)^n \approx 1 + nx$$

$$(1 + R^2/z^2)^{-1/2} \approx 1 - R^2/2z^2$$

$$E_z = \frac{\sigma}{2\epsilon_0} [1 - (1 - R^2/2z^2)] = \frac{\sigma}{2\epsilon_0} \frac{R^2}{2z^2} \quad \sigma = q/A = q/\pi R^2$$

$$E_z = \frac{1}{4\pi\epsilon_0} \frac{q}{z^2} \rightarrow E \text{ from a point charge}$$

→ Final Exam review problem 3

Problem 6

In the figure below, a circular loop of wire is concentric with a solenoid and lies in a plane that is perpendicular to the solenoid's central axis. The circular loop had a radius of 6.00 cm and a resistance of 1.0 mΩ. The solenoid has a radius 2.00 cm, consists of 8000 turns per meter, and carries a current that varies with time according to $i = (0.50 \text{ A/s}) t$. What is the induced current in the circular loop?



$$\begin{aligned}\Phi_B &= \int \vec{B} \cdot d\vec{A} = \int B dA \cos 0^\circ \\ &= B \int dA = BA\end{aligned}$$

for a solenoid $\rightarrow B = \mu_0 n i$

$A = \pi r^2$ * note r is radius of solenoid not circular loop because A is area within the $\vec{B}$ -field

$$\Phi_B = \mu_0 n i (\pi r^2)$$

$$\begin{aligned}\frac{d}{dt} [(0.50 \text{ A/s}) t] &= \\ (0.50 \text{ A/s})\end{aligned}$$

$$|\mathcal{E}| = \frac{d\Phi_B}{dt} = \frac{d}{dt} [\mu_0 n i \pi r^2] = \mu_0 n \pi r^2 \frac{di}{dt}$$

$$= \mu_0 n \pi r^2 (0.50 \text{ A/s})$$

$$= (1.26 \times 10^{-6} \text{ Tm/A}) (8000 \text{ m}^{-1}) \pi (0.02 \text{ m})^2 (0.50 \text{ A/s})$$

$$|\mathcal{E}| = 6.3 \times 10^{-6} \text{ V}$$

$$i = \mathcal{E}/R = \frac{6.3 \times 10^{-6} \text{ V}}{1.0 \times 10^{-3} \Omega}$$

$$\rightarrow i = 6.3 \text{ mA}$$

$$(Tm/A) \left(\frac{1}{m} \right) (m^2) \left(\frac{A}{s} \right)$$


$$Tm^2/s \quad T = N/Am$$

$$(N/Am) \left(\frac{m^2}{s} \right) = \frac{Nm}{As} = \frac{J}{C} = V$$

Problem 4

$$q_{\text{point charge}} = +0.50 \mu\text{C}$$

$$q_{\text{sphere}} = +1.0 \mu\text{C}$$

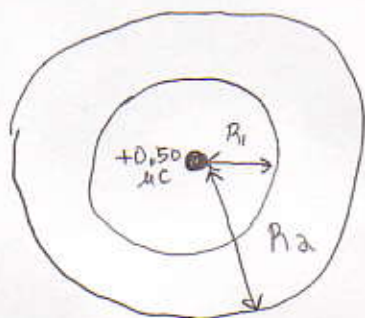

$$q_{\text{inner}} = -0.50 \mu\text{C}$$

$$q_{\text{outer}} = 1.50 \mu\text{C}$$


$$0 < r < R_1) \quad \oint \vec{E} \cdot d\vec{A} = q_{\text{enc}}/\epsilon_0 \rightarrow E(4\pi r^2) = q/\epsilon_0 \quad q = q_{\text{point charge}}$$

$$E = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2} \quad q = +0.50 \mu\text{C}$$

$$R_1 < r < R_2) \quad E = 0 \quad \oint \vec{E} \cdot d\vec{A} = q_{\text{enc}}/\epsilon_0 \quad q_{\text{enc}} = 0 = \overset{+0.50 \mu\text{C}}{q_{\text{point charge}}} + \overset{-0.50 \mu\text{C}}{q_{\text{inner}}}$$

$$r > R_2) \quad E = \frac{1}{4\pi\epsilon_0} \frac{q_{\text{enc}}}{r^2} \quad q_{\text{enc}} = q_{\text{point charge}} + q_{\text{sphere}} = +1.50 \mu\text{C}$$

$$V_{\text{point charge}} = \frac{1}{4\pi\epsilon_0} \frac{q}{r} = V_{\text{sphere}} \quad E_r = -\frac{\partial V}{\partial r}$$

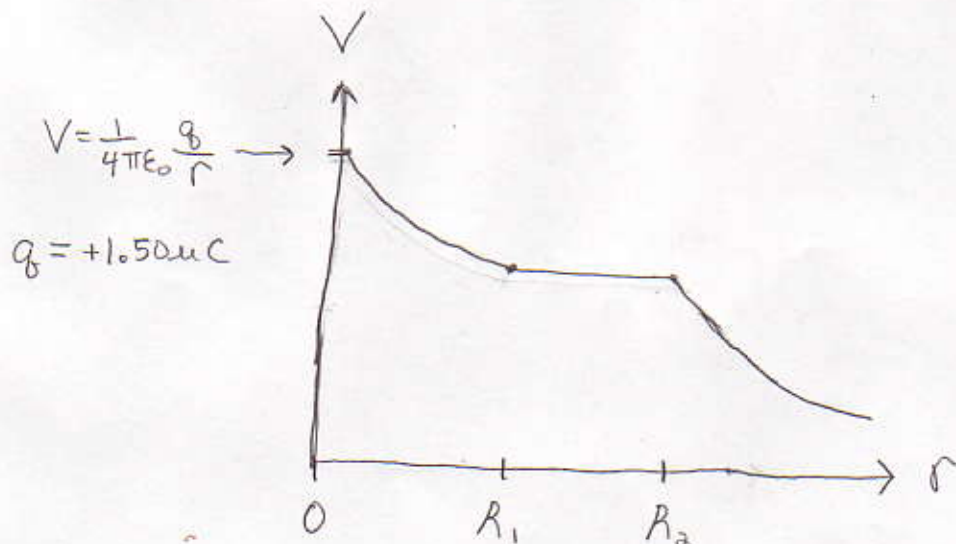

Problem 5

$$\left. \begin{array}{l} C_2 = 1.0 \mu\text{F} \\ q_2 = 10 \mu\text{C} \end{array} \right\} V_2 = q_2 / C_2 \rightarrow \frac{10 \mu\text{C}}{1.0 \mu\text{F}} = 10.0 \text{V}$$

$V_3 = V_2 = 10.0 \text{V}$ since capacitors are in parallel

$$q_3 = C_3 V_3 = (4.0 \mu\text{F})(10.0 \text{V}) = \boxed{40 \mu\text{C} = q_3}$$

$$q_{23} = q_2 + q_3 = 50.0 \mu\text{C}$$

$\Rightarrow$ in series, q is same $q_1 = q_{23} \rightarrow \boxed{q_1 = 50 \mu\text{C}}$


$$V_1 = q_1 / C_1 = 50 \mu\text{C} / 2 \mu\text{F} = 25 \text{V}$$

$$E = V_1 + V_{23} = \boxed{35 \text{V}}$$

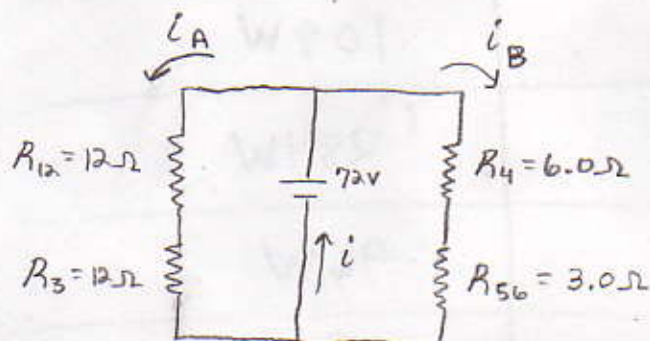Problem 6

$$1/R_{12} = 1/R_1 + 1/R_2 \rightarrow R_{12} = 12\Omega$$

$$1/R_{56} = 1/R_5 + 1/R_6 \rightarrow R_{56} = 3.0\Omega$$



$$i_B = \frac{72V}{9.0\Omega} = 8.0A$$

$$i_A = \frac{72V}{24\Omega} = 3.0A$$

$$i = i_A + i_B = 11.0A$$

$$i_{12} = i_3 = 3.0A$$

$$V_3 = i_3 R_3 = 36V$$

$$V_{12} = i_{12} R_{12} = 36V \rightarrow V_1 = V_2 = 36V$$

$$i_1 = V_1/R_1 = 1.5A$$

$$i_2 = V_2/R_2 = 1.5A$$

$$i_4 = i_{56} = 8.0A$$

$$V_{56} = i_{56} R_{56} = 24V$$

$$V_4 = i_4 R_4 = 48V$$

$$V_5 = V_6 = 24V$$

$$i_5 = V_5/R_5 = 24V/6\Omega = 4.0A$$

$$i_6 = V_6/R_6 = 24V/6\Omega = 4.0A$$

	current	V_{drop}	P_{avg}
R_1	1.5A	36V	54W
R_2	1.5A	36V	54W
R_3	3.0A	36V	108W
R_4	8.0A	48V	384W
R_5	4.0A	24V	96W
R_6	4.0A	24V	96W
E	11.0A	72V	792W